

* BASIC *


9784236981

SUBJECT -

TOPIC

P. No: 3

* POWER *

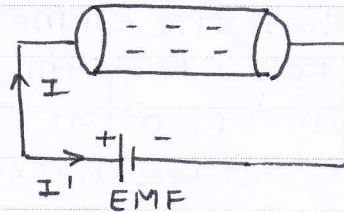

$I' \rightarrow$ Natural current
 $I \rightarrow$ Conventional current

\rightarrow The flow of electron is called as current or the time rate of charge is also called as current

$$I = \frac{dQ}{dt} \quad \text{C/s or Amp} \quad Q_e = -1.602 \times 10^{-19} \text{ C}$$


\rightarrow To move e^- for one point to another point external force required is called EMF (V)

$$V = \frac{dW}{dQ} \quad \text{J/C or volt}$$

\rightarrow The time rate of energy called as power.


$$P = \frac{dW}{dt} \quad \text{J/sec or watt} = \frac{dW}{dQ} \cdot \frac{dQ}{dt} = V \cdot I$$

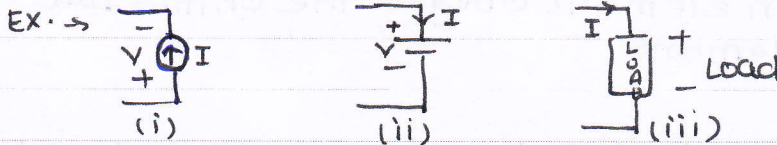\rightarrow When current enter positive terminal element absorbing power.



All diagram absorb power.

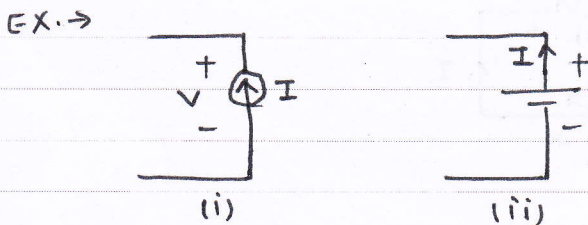\rightarrow When current leaving from positive terminal called element deliver power.



\rightarrow The capacity to do work called ENERGY

$$W = \int_0^t P \cdot dt \quad \text{Watt-sec or Joule.}$$

\rightarrow ANY CKT power Absorb = power Drivers.

* CLASSIFICATION OF ELEMENTS :->

* Active element :- when the element is capable of delivering energy independently for a long time (approx) or having property of internal amplification called Active element.

Example :- (i) Independent voltage and current source

(ii) Dependent Transistor or op-Amp source

-> during discharge capacitor can deliver energy at short time not a long time so it is not Active element.

* passive element :-> when the element is not capable of delivering

energy independently the element called passive element.

Example :- R, Bulb, Transformer, ($V_1 I_1 = V_2 I_2$)


CMT ** IF V/I ratio \oplus in both direction called passive else Active **

* Bidirectional element :-> when element have properties & characteristic are independent on the direction of current called bi-directional (Bi-lateral) element.



CMT ** When opposite coordinate figure same than Bidirectional else Uni-Di.

* Linear element :-> when element obey's the ohm's Law. the element called linear element

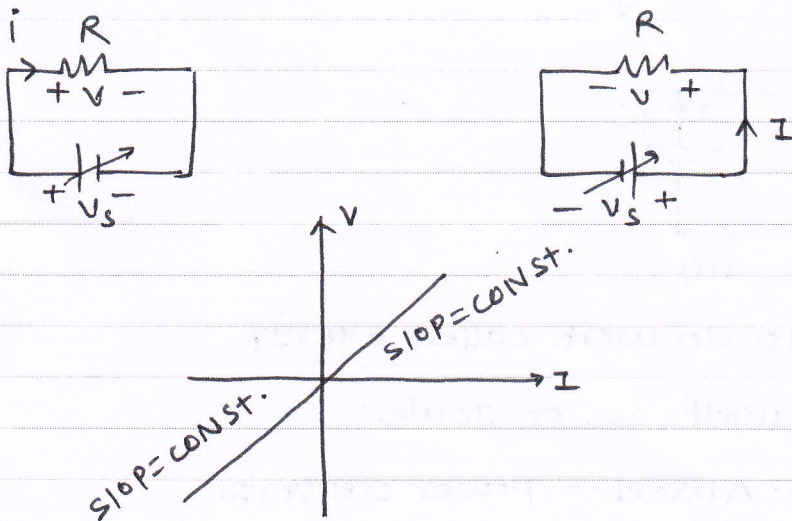CMT ** Every linear element have Bidirectional property but not vice-versa **



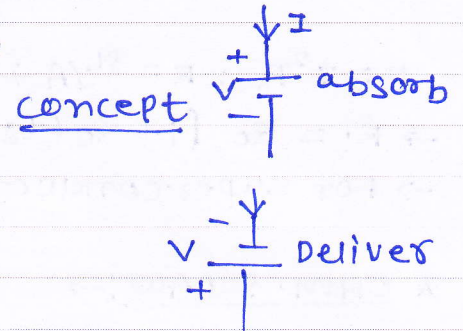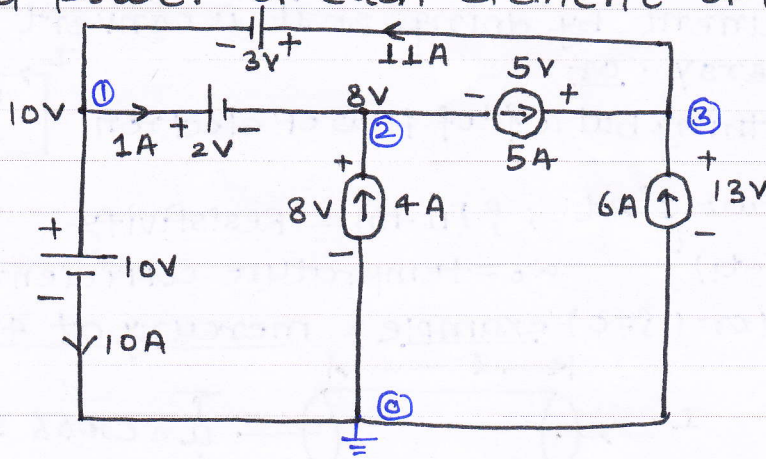Q.1. Find power of each element of Network shown




- AUS:-
- $P_{10} = 10 \times 10 = 100 \text{ watt (absorb)}$
 - $P_{12} = 2 \times 1 = 2 \text{ watt (absorb)}$
 - $P_{23} = 5 \times 5 = 25 \text{ watt (deliver)}$
 - $P_{13} = 11 \times 3 = 33 \text{ watt (absorb)}$
 - $P_{20} = 8 \times 4 = 32 \text{ watt (Deliver)}$
 - $P_{30} = 13 \times 6 = 78 \text{ watt (deliver)}$
- Total power absorb $(100 + 2 + 33 = 135 \text{ watt}) =$
 Total power Deliver $(32 + 78 + 25 = 135 \text{ watt})$

Q.2. IDENTIFY GIVEN figure type OF ELEMENT.

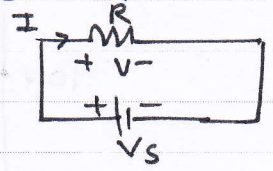- (a) \rightarrow passive ($V/I \oplus$ 1 & 3 Quad.)
 \rightarrow unidirectional (not same fig 1 & 3 Quad.)
 \rightarrow non linear (slop not const.)
- (b) \rightarrow passive ($V/I \oplus$ 1 & 3 Quad.)
 \rightarrow Bidirectional (same fig 1 & 3 Quad.)
 \rightarrow non linear (slop not const.)
- (c) \rightarrow Active ($V/I = \ominus$ 2 & 4 Quad.)
 \rightarrow Bidirectional (same fig 2 & 4 Quad.)
 \rightarrow Linear (slop const.)
- (d) \rightarrow Active ($V/I \oplus$ 1st & 2nd Quad.)
 \rightarrow non linear (slop not const.)
 \rightarrow unidirectional (not same fig. in opposite quad.)

* Resistance * Resistor is a property of Resistor is always oppose a current by doing. so it is convert electrical energy to Heat energy. or
Resistance is nothing but a f^m of flow of electron



$$P = I^2 R ; R = \rho L/A ; W = I^2 R t ; \rho (\Omega\text{-m}) = \text{Resistivity}$$

$$\rightarrow R_1 = R_0 [1 + \alpha_0 (t_2 - t_1)] \quad \alpha_0 = \text{temperature coefficient}$$

\rightarrow For superconductor ($\rho = 0$) example: mercury at 4.15 K temp.


* OHM'S LAW: \rightarrow $a = \text{cross sectional Area.}$

Ohm's Law state that constant temp. and conductivity of material constant current density is directly proportional to electric field intensity. $J \propto E \Rightarrow J = \sigma E \Rightarrow I/a = \frac{1}{\rho} \cdot \frac{V}{l}$

CMT $\rightarrow \boxed{\frac{V}{I} = \frac{\rho l}{a} = R ; J = \frac{I}{a} ; E = \frac{V}{l} ; \sigma = \frac{1}{\rho} \text{ mho/m or } (\Omega\text{-m})^{-1}}$

or

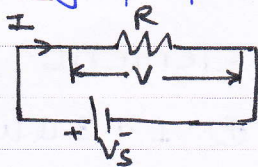ohm's low state that potential difference across the element is directly proportional to current following to element.



$$V \propto I \Rightarrow V = IR \Rightarrow R = \frac{V}{I} = \text{const.}$$

$I \propto V_s$ (EMF) or V (Voltage drop / P.D) $\propto I$ Both statement valid.

- (i) EMF independent on current and resistor magnitude
- (ii) potential difference depend on current & Resistor magnitude

* ELECTRICAL circuit

$$\rightarrow I = \frac{V}{R} = \frac{\text{EMF}}{R}$$

$$\rightarrow I = \frac{V}{R} = \frac{V}{\rho l/a} = \frac{\text{EMF}}{\rho l/a}$$

* magnetic circuit

$$\rightarrow \phi = \frac{\text{MMF}}{S (\text{Reluctance})}$$

$$\rightarrow \phi = \frac{NI}{l/a \mu_0 \mu_r}$$


$$\rightarrow L = \frac{N^2 \mu_0 \mu_r a}{l} = \frac{N^2}{l/a \mu_0 \mu_r} = \frac{N^2}{S}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m} ; \mu_r = 1 \text{ air}$$

\rightarrow permeability is the property of medium. $l = \text{length of core}$; $a = \text{Area of cross sectional}$ which magnetic field exist.

* Faraday Law :->

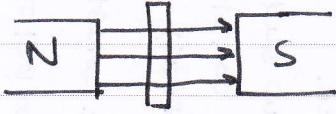* First Law :-> When conductor cuts a magnetic lines of force an emf induced in the conductor.






* second Law :-> EMF induced in the conductor is directly proportional to rate of change of Flux.

$$e \propto \frac{d\phi}{dt} \Rightarrow e = BLV \sin \theta$$

CMT * $\rightarrow e =$ Dynamic Induced emf (Generator)

$B =$ Flux density, $l =$ length of conductor, velocity of conductor - V

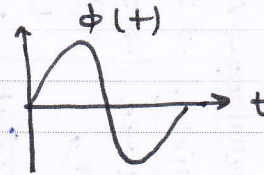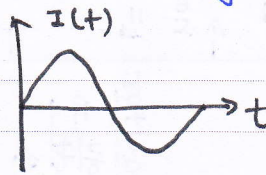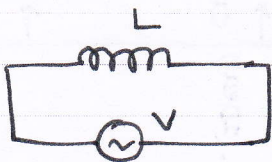$\theta =$ Angle b/w conductor & magnetic line.



$$e \propto \frac{d\phi}{dt}$$

CMT * $e = -N \frac{d\phi}{dt}$ = statically induced emf (Transformer).

\rightarrow due to Lenz's Law

CMT * Flux linkage $\psi = N\phi = LI$

$$V = \frac{d\psi}{dt} = N \frac{d\phi}{dt}$$

$$v = L \frac{di}{dt}$$

Inductor (L)


$\rightarrow LI = N\phi$
 $\rightarrow V = L \frac{di}{dt} \Rightarrow I = \frac{1}{L} \int_{-\infty}^t V \cdot dt$
 $\rightarrow P_{INST.} = V \cdot I = L \frac{di}{dt} \cdot I \Rightarrow W = \int P_{INST.} dt = \frac{1}{2} LI^2$

- \rightarrow Avg. power dissipation in ideal inductor zero
- \rightarrow Inductor store energy in form magnetic field (K.E).
- \rightarrow Inductance independent on current magnitude called linear inductor or air core inductor



- $L = \frac{V}{di/dt} = \text{const.}$
- $I \uparrow 10\% \rightarrow \phi \uparrow 10\%$
- $I \uparrow 90\% \rightarrow \phi \uparrow 90\%$
- \rightarrow Depend on current magnitude called non linear or iron core inductor.
- $L = \frac{N\phi}{I}$; $V \uparrow$ saturation $\phi \uparrow$ saturation.
- \rightarrow Under steady state for DC source act short circuit. $V = L \frac{di}{dt} \Rightarrow V = 0$.


- \rightarrow Inductor does not allow sudden change of current bcs if required ∞ voltage (practical).
- $V = L \frac{di}{dt} |_{dt \rightarrow 0} = \infty$ (ideal)

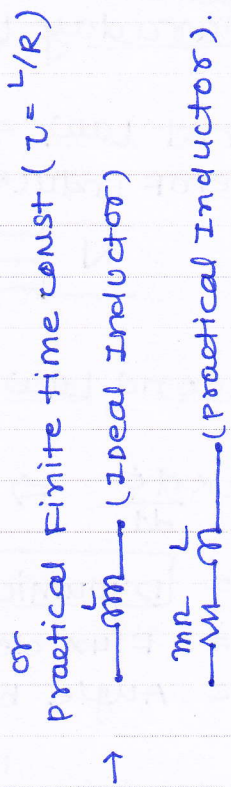

Capacitor (C)


$\rightarrow Q = CV \Rightarrow C = \frac{Q}{V} \left\{ \frac{\text{Coulomb}}{\text{Volt}} \text{ or Farad} \right\}$
 $\rightarrow I = \frac{dQ}{dt} = C \frac{dV}{dt} \Rightarrow V = \frac{1}{C} \int_{-\infty}^t I \cdot dt$
 $\rightarrow P = V \cdot I = V \cdot C \frac{dV}{dt} \Rightarrow W = \int P \cdot dt = \frac{1}{2} CV^2$

- \rightarrow Avg. power dissipation in ideal capacitor equal zero
- \rightarrow Capacitor store energy in form electric field.
- \rightarrow When capacitance is independent on voltage magnitude called linear capacitor.
- $C = \frac{Q}{V} = \text{const.}$ $\therefore V \uparrow 10\% \therefore Q \uparrow 10\%$
- \rightarrow When it depend on voltage magnitude called non linear capacitor! - ex: - varactor diode
- $C = Q/V = \text{variable}$

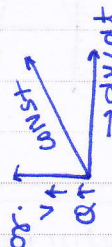





- \rightarrow steady state condition for DC source capacitor Act AS open circuit $\Rightarrow I = C \frac{dV}{dt}$
- \rightarrow capacitor does not allow sudden change of voltage if voltage bcs sudden change of voltage if required infinite current $I = C \frac{dV}{dt} |_{dt=0} ; I = \infty$ (ideal) (practical) :- Finite time constant ($\tau = RC$)

- \rightarrow capacitor does not allow sudden change of voltage if voltage bcs sudden change of voltage if required infinite current $I = C \frac{dV}{dt} |_{dt=0} ; I = \infty$ (ideal) (practical) :- Finite time constant ($\tau = RC$)

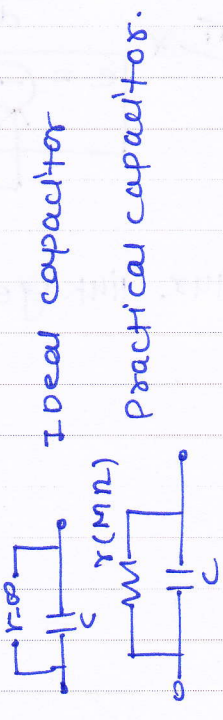


* Voltage source :->

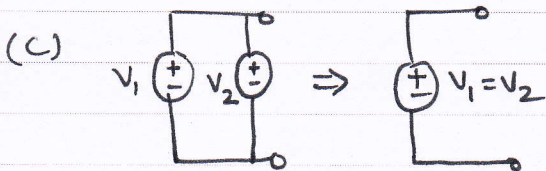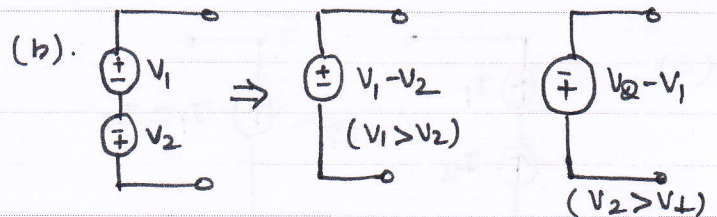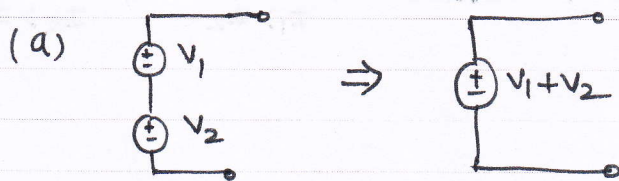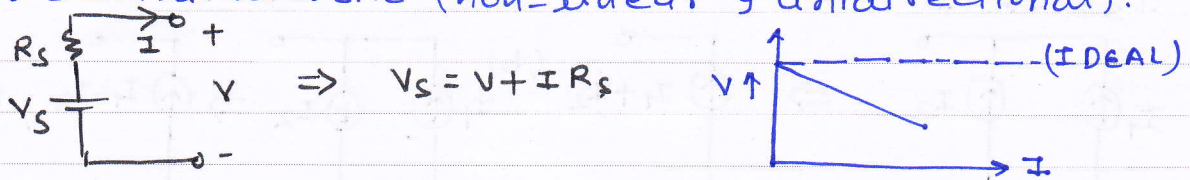
- (i) Ideal voltage source delivers energy at specify voltage (V) which is independ on current Delivers by source.
- (ii) Internal Resistance of ideal voltage source = zero. ($R_s=0$).
- (iii) practical voltage source delivers energy as specify voltage which depend on current Delivers by source.
- (iv) Independent voltage source does not obey ohm's law. V-I characteristic (non-linear & unidirectional).




Q. Find current in 2Ω Resistor?

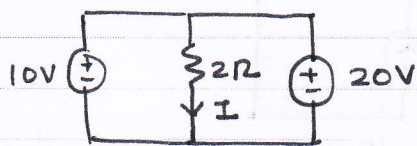

$10 \neq 20$
NOT satisfied KVL.

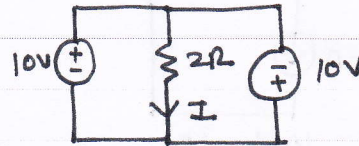

$10 \neq -10$
NOT satisfied KVL


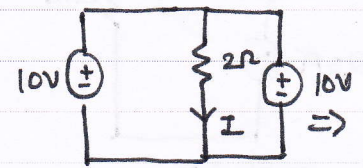


$10 = 10$ So $I = \frac{10}{2} = 5A$
satisfied KVL








*** current source ***

- (i) Ideal current source deliver energy at specified current (I) which is independent on voltage across the source
- (ii) Internal resistance of Ideal current source = infinite.


(iii)

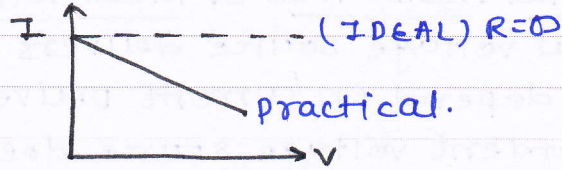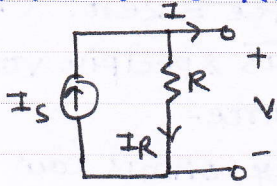

$I_s = IR + I$

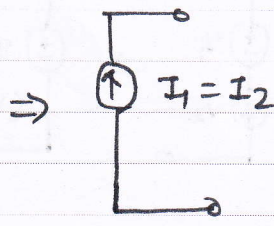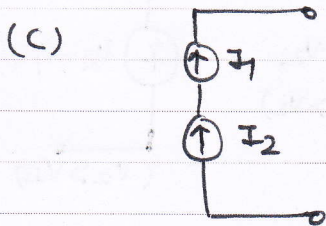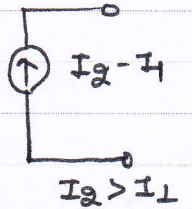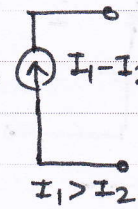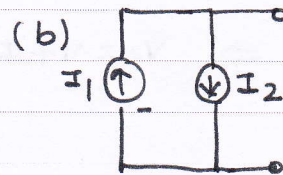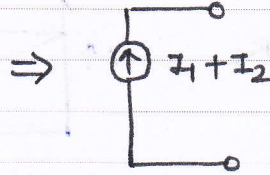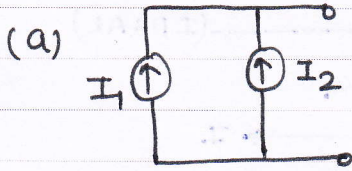


Q. Find current I in 2Ω resistor?

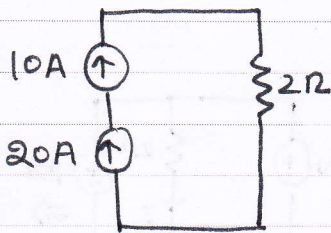


$10 \neq 20$

NOT USE KCL

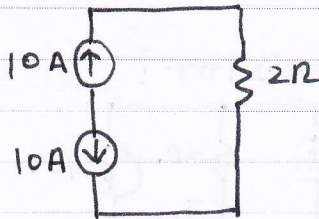

$10 \neq -10$


NOT USE KCL

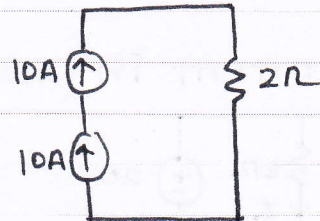

$10 = 10$

USE KCL so $I = 10A$ at 2Ω .

* KCL (Law of Conservation Charge) :->

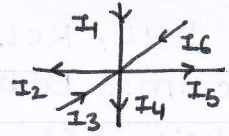


(i) algebraic sum of current = 0 at a point.

(ii) When two point element connect common point called simple Node or more than two element called principal Node.


(iii) $I_1 + I_3 + I_6 = I_2 + I_4 + I_5$

(iv)

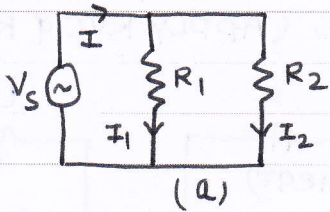


$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$

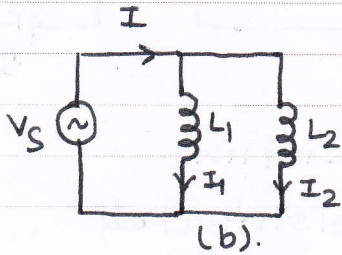$I_1 = \frac{I \cdot R_2}{R_1 + R_2}$; $I_2 = \frac{I \cdot R_1}{R_1 + R_2}$



$L_{eq} = \frac{L_1 \cdot L_2}{L_1 + L_2}$

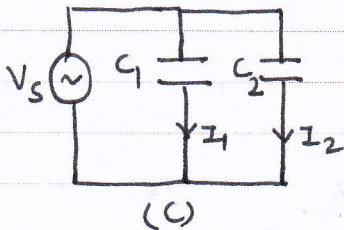$I_1 = \frac{I \cdot L_2}{L_1 + L_2}$; $I_2 = \frac{I \cdot L_1}{L_1 + L_2}$




$C_{eq} = C_1 + C_2$


$I_1 = \frac{I \cdot C_1}{C_1 + C_2}$; $I_2 = \frac{I \cdot C_2}{C_1 + C_2}$

* KVL (Law of Conservation Energy) *

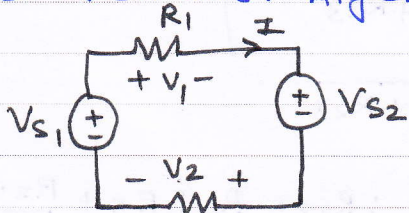(i) statement: Algebraic sum of voltage included closed loop is zero.



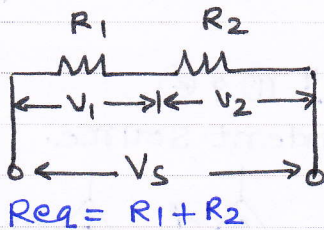
$\Rightarrow V_{s1} = V_1 + V_2 + V_{s2}$



$R_{eq} = R_1 + R_2$

$V_1 = \frac{V_s \cdot R_1}{R_1 + R_2}$


$V_2 = \frac{V_s \cdot R_2}{R_1 + R_2}$

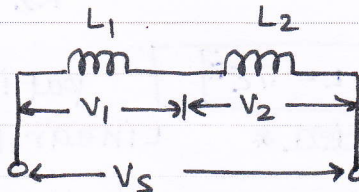

$L_{eq} = L_1 + L_2$

$V_1 = \frac{V_s \cdot L_1}{L_1 + L_2}$

$V_2 = \frac{V_s \cdot L_2}{L_1 + L_2}$

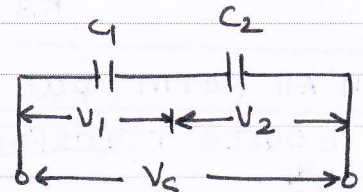



$C_{eq} = (C_1 || C_2) = \frac{C_1 \cdot C_2}{C_1 + C_2}$

$V_1 = \frac{V_s \cdot C_2}{C_1 + C_2}$


$V_2 = \frac{V_s \cdot C_1}{C_1 + C_2}$

- KVL, KCL Fails For distributed parameter
- Ohm's Law apply lumped or distributed parameter
- KVL, KCL Apply [Lumped + linear/non linear + uni or bi Directional. + Time variant or time invariant]

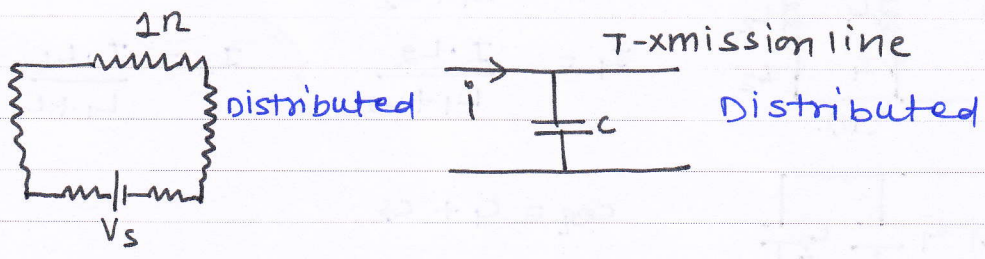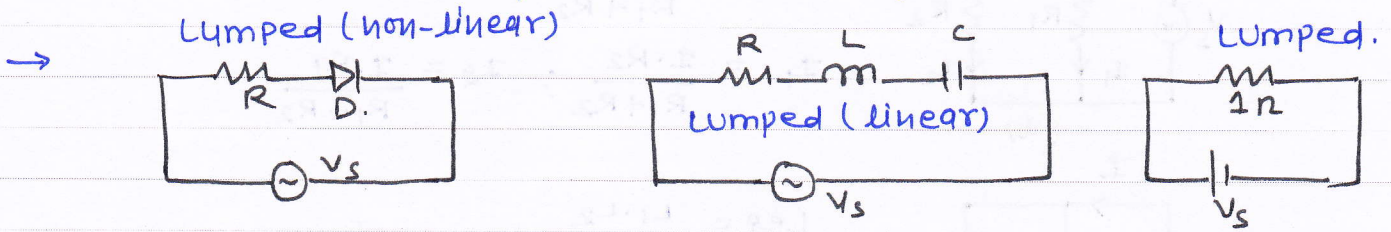- * Field theory → Apply Low & High Frequency (Not Apply KVL & KCL)
- * Network theory → Low Frequency (Apply KVL & KCL).



* Y-Δ CONVERSION *

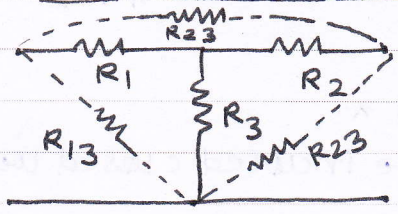

Δ to Y.

$$R_1 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_3 = \frac{R_{23} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$


①

Y to Δ


$$R_{12} = R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3}; R_{13} = R_1 + R_3 + \frac{R_1 \cdot R_3}{R_2}; R_{23} = R_2 + R_3 + \frac{R_2 \cdot R_3}{R_1} \quad \text{--- ②}$$

IN All Form put $[R=L=1/c^2]$



* SOURCE TRANSFORMATION *

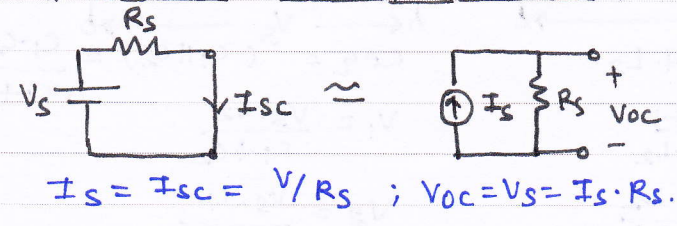









Linear dependent source.

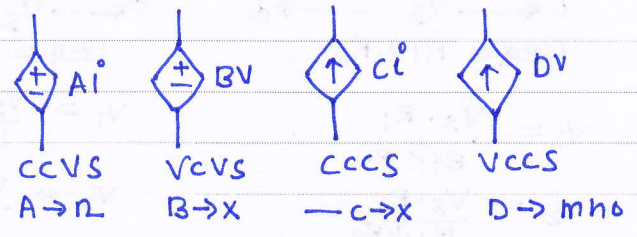


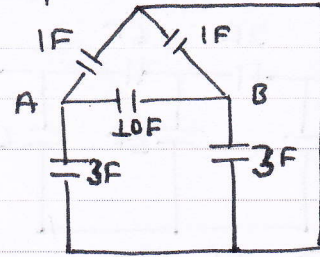
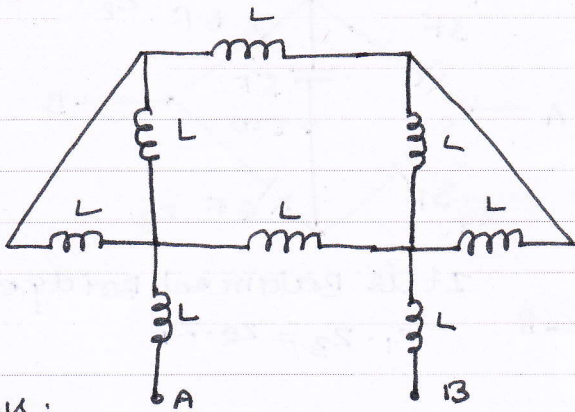
Q.3. Find equal Inductance or capacitance between A & B is



ANS:-

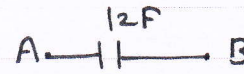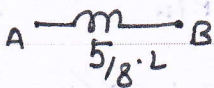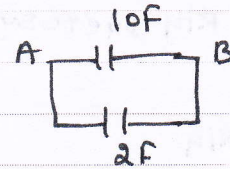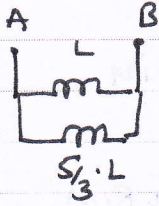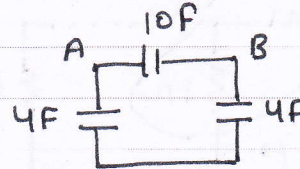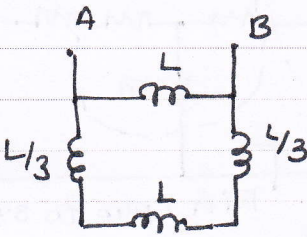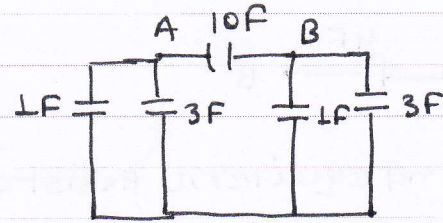
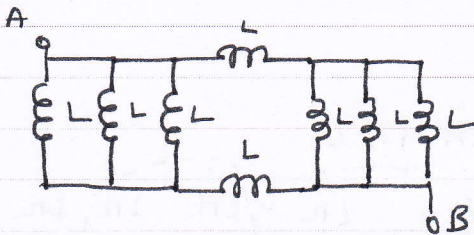


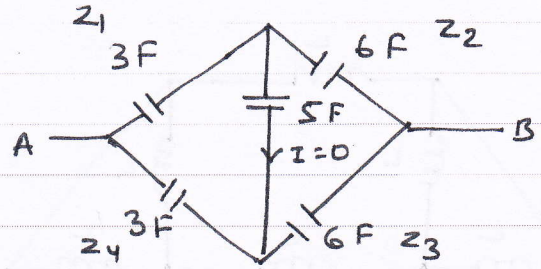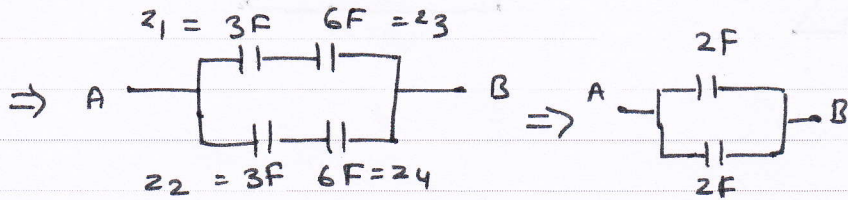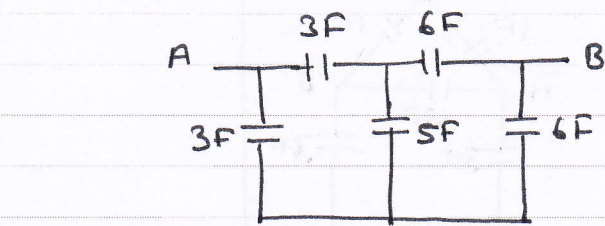Q.4. Find equivalent capacitance b/w A & B.



It is balanced bridge so $z_1 \cdot z_3 = z_2 \cdot z_4$

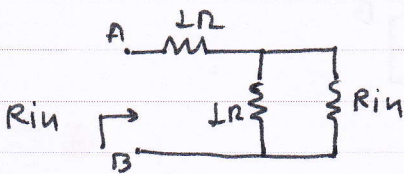
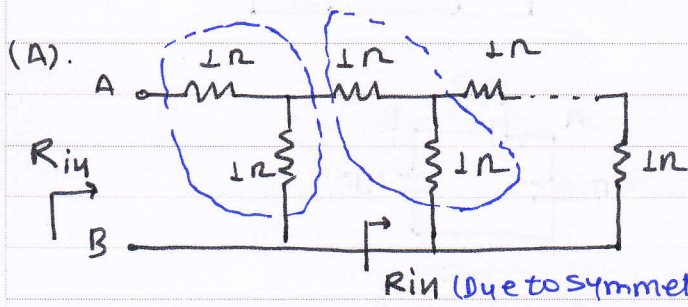
Q.5. Find equivalent resistance between A & B



$$R_{iH} = 1 + \frac{1 \times R_{iH}}{1 + R_{iH}}$$

$$R_{iH}^2 - R_{iH} - 1 = 0$$

$$R_{iH} = \frac{1 + \sqrt{5}}{2} R$$

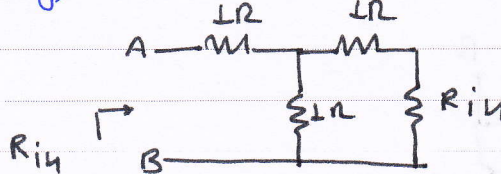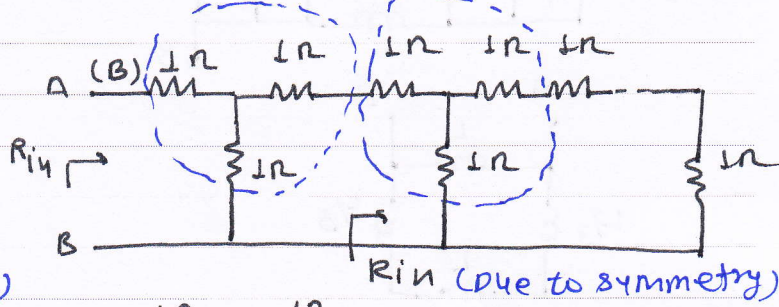


$$R_{iH} = 1 + \frac{1 \times (1 + R_{iH})}{1 + 1 + R_{iH}} = \frac{3 + 2R_{iH}}{2 + R_{iH}}$$

$$2R_{iH} + R_{iH}^2 = 3 + 2R_{iH}$$

$$R_{iH} = \sqrt{3} R$$

Q.6 Find current in 2Ω Resistor?

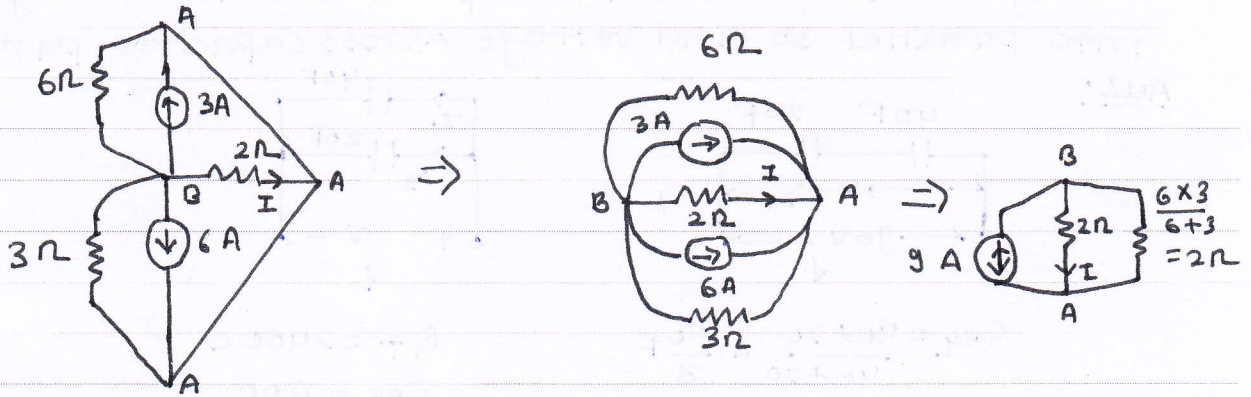


So current divider rule


$$I = \frac{-9 \times 2}{4} = -4.5 \text{ Amp (B} \rightarrow \text{A)}$$

$$I = 4.5 \text{ Amp (A} \rightarrow \text{B)}$$

Q.7. Find the value of I ?

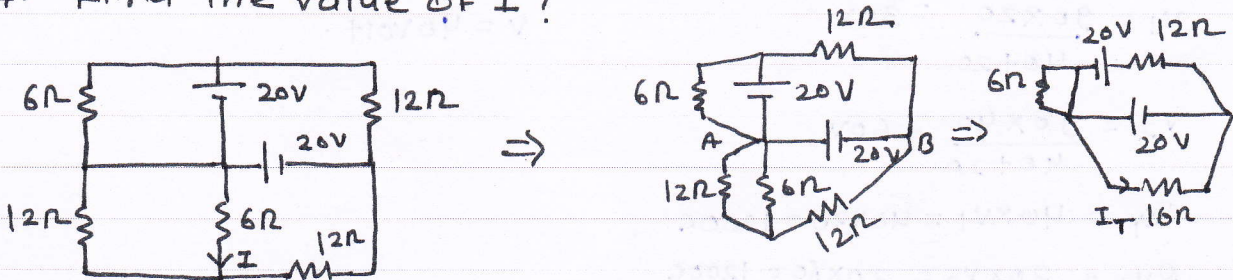


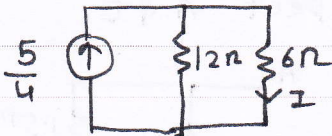Parallel voltage same $I_T = \frac{20}{16} = \frac{5}{4}$ Amp.



$$I = \frac{5 \times 12^3}{18} = \frac{15}{18} = \frac{5}{6} = 0.7 \text{ Amp.}$$



Q.8. Find an energy of given capacitor?

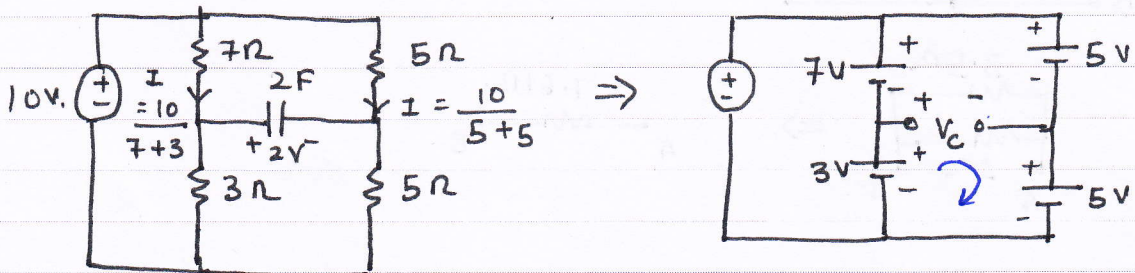

$$-3 + V_C + 5 = 0 \Rightarrow V_C = -2V. ; \text{ capacitor energy} = \frac{1}{2} CV^2 = \frac{1}{2} \times 2 \times 4 = 4 \text{ Watt}$$

Q.9. Two capacitor of 40F & 20F Are connected in series to source voltage of 90V. When two capacitor charged fully & connected into parallel so find voltage across capacitor parallel connection?

Ans:-

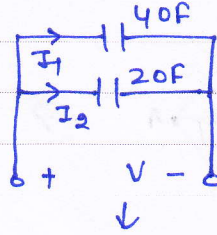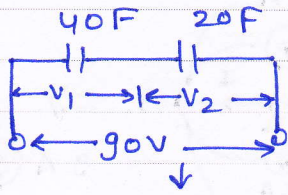

$$C_{eq} = \frac{40 \times 20}{40 + 20} = \frac{40}{3} F$$

$$Q = C_{eq} \cdot V = \frac{40}{3} \times 90$$

$$Q = 1200 C$$

$$V_1 = \frac{90 \times 20}{40 + 20} = 30 V$$

$$V_2 = \frac{90 \times 40}{40 + 20} = 60 V$$

$$Q_{V_1} = 40 \times V_1 = 40 \times 30 = 1200 C$$

$$Q_{V_2} = 20 \times V_2 = 20 \times 60 = 1200 C$$

$$Q_T = Q_{V_1} + Q_{V_2} = 2400 C$$

$$Q_T = 2400 C$$


$$C_{eq} = 60 F$$

$$Q_T = C_{eq} \cdot V$$


$$2400 = 60 \times V$$

$$V = 40 \text{ Volt}$$


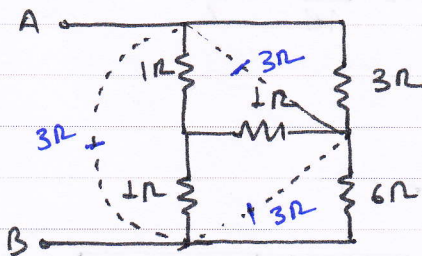
Q.10. Find equivalent Resistance with respect A & B.




\Rightarrow

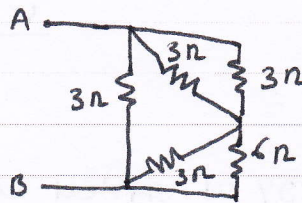

\Rightarrow

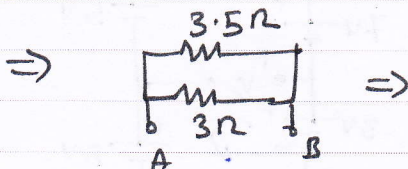
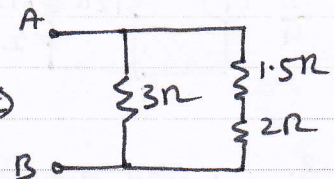


\Rightarrow

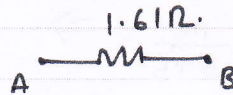

* Mesh Analysis :->

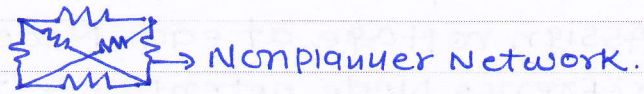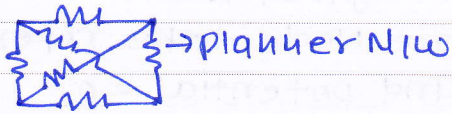- > mesh Analysis can be Applied only for planer Network
- > A Network Have NO cross connection its diagonal element called planer Network




-> NO OF KVL or mesh equation = $e = b - N + 1 = b - N + 1 = b - (N - 1)$
 (N = principal Node.)

* procedure *

- Identify total NO OF Mesh in the given Network by $e = b - (N - 1)$
- assign current direction for each mesh (clockwise) $\rightarrow I$
- devlop KVL eqⁿ for each mesh.
- By solving KVL eqⁿ find loop current.

ex:->

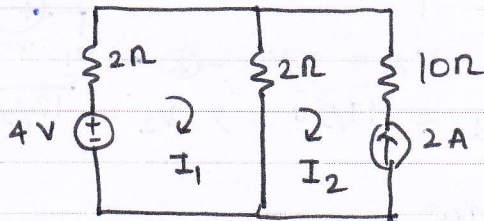

$N = 2, b = 3$


- NO OF mesh eqⁿ = $b - (N - 1) = 3 - (2 - 1) = 2$
- take direction of current in loop clockwise
- APPLY KVL in 1st loop & 2nd loop
 $-4 + 2I_1 + 2(I_1 - I_2) = 0$ - ①
 $10I_2 + 2(I_2 - I_1) = 0$ - ②
 $I_3 = -2A$ - ③

So solution eqⁿ ①, ② & ③ $I_2 = -2A, I_1 = 0A.$

* Supermesh * When current source branch is common for two mesh. it is possible to find solution super mesh technique.

cmT * *
 Mesh = KVL + Ohm's Law
 Supermesh = KVL + KCL + Ohm's Law

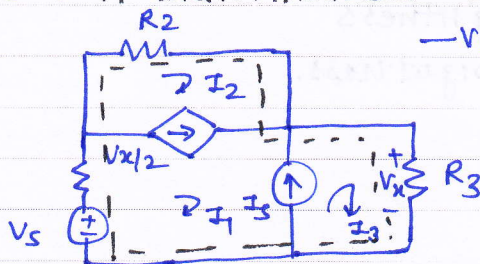Ex: devlop mathematical eqⁿ for Network shown



$-V_s + R_1 I_1 + R_2 I_2 + R_3 I_3 = 0$ (KVL)

$I_1 - I_2 = \frac{V_x}{2}$ (KCL)

$I_1 - I_3 = -I_s$ (KCL)

* Nodal Analysis *

→ It can applied linear or non linear or planar network

* procedure :->

- (a) Identify total NO of nodes in the given network = $e = (N-1)$
- (b) Assign voltage at each Node one Node take reference Node
→ reference Node potential = ground potential = 0
- (c) Devlop KCL equation of each non-reference Node.
- (d) solving KCL equation find Node voltages.

* Super Node * When Ideal voltage source connected between two non-reference Node and find soln by super Node method.

ex:-

so V_1 & V_2 common point due to super Node

$$\frac{V_1}{1} + \frac{V_2}{1} = 10 + 5 \quad \text{--- (1)}$$


$$V_1 - V_2 = 2V \quad \text{--- (2)}$$

$$V_1 = 17/2V \quad ; \quad V_2 = 13/2V.$$


Node = KCL + Ω Law
 Super Node = KCL + KVL + Ω Law

* Bulb brightness *

series connected Bulb

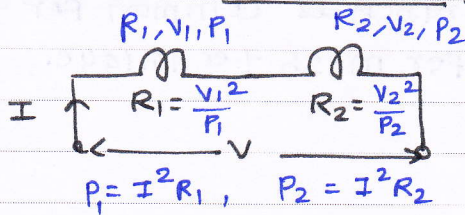


parallel connected Bulb

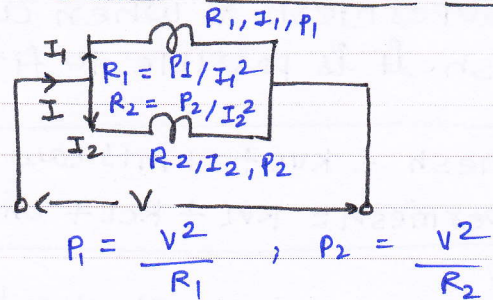

When voltage Rating same:-

- (a) series low rating Bulb more Brightness
- (b) parallel High rating Bulb more Brightness.

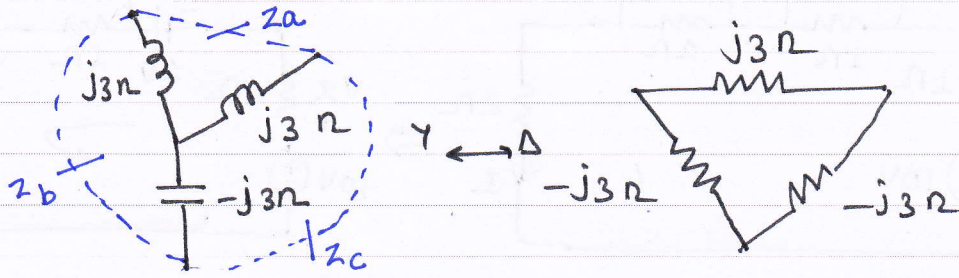Q.12. Identify element Y-Δ conversion given connection.







$$Z_a = j3 + j3 + \frac{j3 \times j3}{-j3} = j3\Omega \text{ (Inductor)}$$


$$Z_b = j3 - j3 + \frac{j3 \times -j3}{j3} = -j3\Omega \text{ (capacitor)}$$

$$Z_c = j3 - j3 + \frac{j3 \times -j3}{j3} = -j3\Omega \text{ (capacitor)}$$

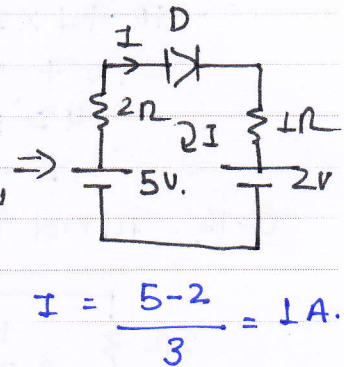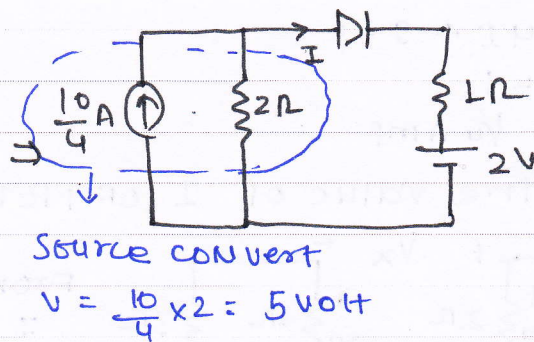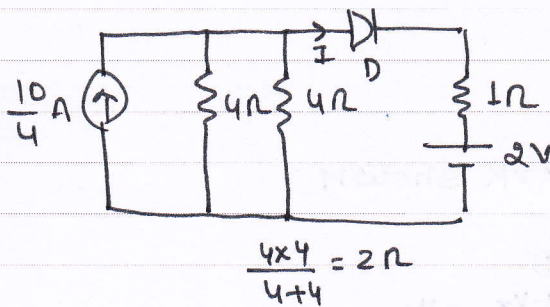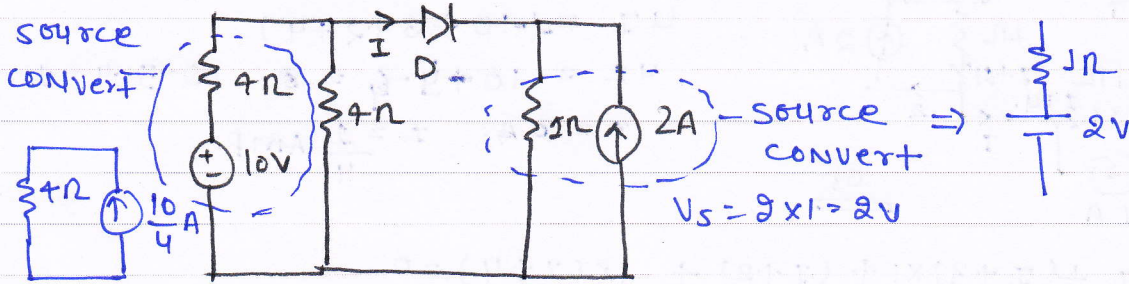Q.13. Find current through ideal diode is: $I = ?$



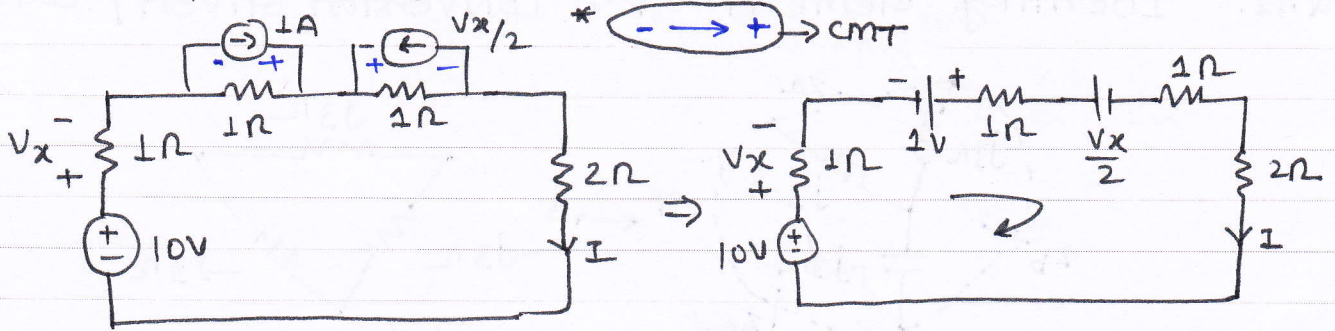Q.14. Find current of 2Ω Resistor on given N/w




$$-10 + 5I - 1 + \frac{V_x}{2} = 0 ; \quad V_x = I$$

$$-10 + 5I - 1 + \frac{I}{2} = 0$$

$$I = 2A$$

* Good

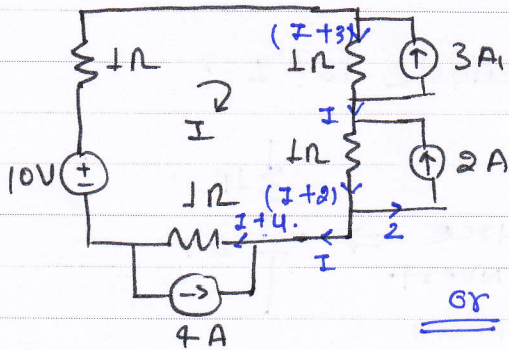Q.15 Find the value of I of the Network shown!



$$-10 + 1 \times I + I + 3 + I + 2 + I + 4 = 0$$

$$4I = 1$$

$$-10 + 4 \times I + (1 \times 3) + [I \times 2] + (1 \times 4) = 0$$

$$4I = -(-10 + 3 + 2 + 4)$$

$$4I = 10 + 5 - 6 = 9 \quad 10 - 5 - 4 = 1$$

$$I = \frac{1}{4} \text{ Amp.}$$


$$-10 + 1 \times I + (I + 3) \times 1 + (I + 2) + 1 \times (I + 4) = 0$$

$$-10 + 4I + 9 = 0$$

$$4I = 1$$

$$I = \frac{1}{4} \text{ Amp}$$

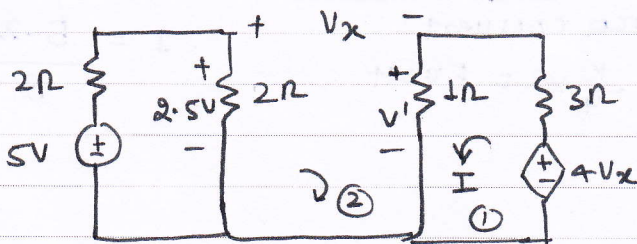Q.16. Find the value of I of Network shown.



From ①

$$I = \frac{4V_x}{4} = V_x$$


$$V_1 = 1 \times I = I$$

From ② $-2.5 + V_x + I = 0$

$$2I = 2.5$$

$$I = 1.25 A.$$

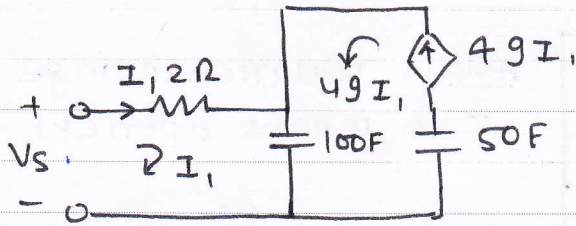Q.17. Find equivalent capacitance w.r.t A & B




$$V_s = 2I_1 + \frac{1}{100} \int 50I_1 dt$$

$$V_s = 2I_1 + \frac{1}{2} \int I_1 dt \quad \text{--- (1)}$$

$$\text{General eq}^n V_s = RI + \frac{1}{C_{eq}} \int I_1 dt \quad \text{--- (2) compare } \boxed{C_{eq} = 2F}$$

Q.18. A practical DC source of 3V with internal resistance of 2Ω is connected to non linear resistor. the characteristic of non linear resistor given by $V_{NL} = I_{NL}^2$ Find power dissipation in non-linear resistor?

Ans:-

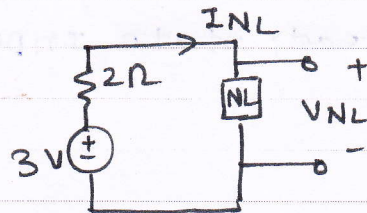

$$-3 + 2I_{NL} + V_{NL} = 0$$


$$-3 + 2I_{NL} + I_{NL}^2 = 0$$

$$I_{NL} = -3A, 1A$$

power dissipation (power absorb) \uparrow so $I_{NL} = 1A$

$$P_{NL} = V_{NL} \times I_{NL} = I_{NL}^3 = 1 \text{ watt}$$

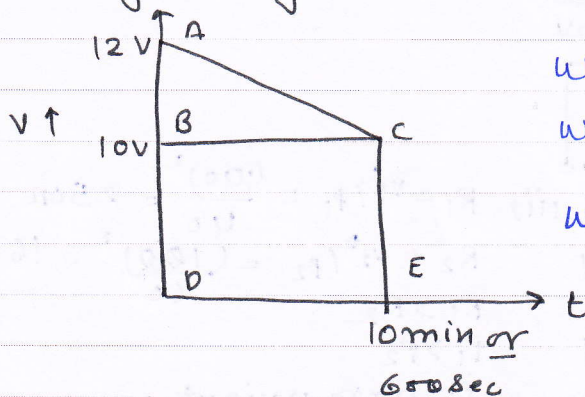Q.19 A fully charged mobile is good for 10min talk time during battery delivers a constant current of 2amp. Find energy of the battery during talktime in given characteristic:




$$W = (\Delta ABC + \square BCDE) \times 2$$


$$W = \left(\frac{1}{2} \times 600 \times 2 + 10 \times 600 \right) \times 2$$

$$W = 6600 \times 2 = 13.2 \text{ kJ}$$

Q.20. Find the value of I shown Fig.

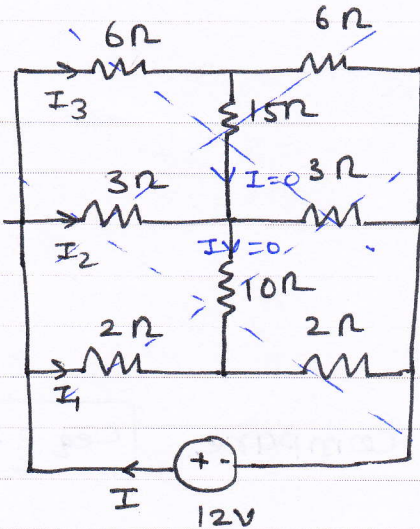


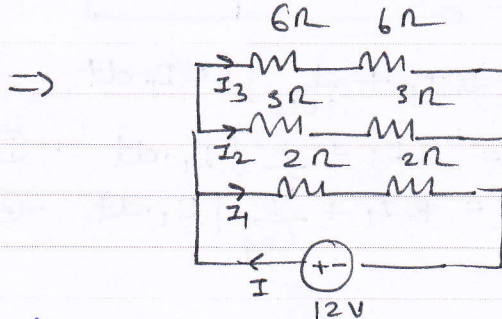Ans:- Balance Bridge
 $I = 0$ means open ckt




$$I = I_1 + I_2 + I_3 = \frac{12}{6+6} + \frac{12}{3+3} + \frac{12}{2+2} = 1 + 3 + 2 = 6 \text{ A.}$$

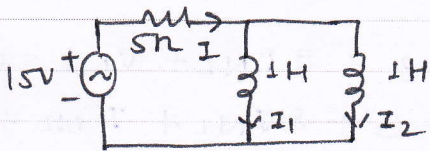Q.21 Find steady state current I_1, I_2 in steady state condition.




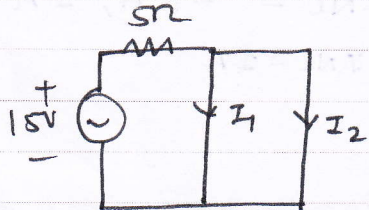
at steady state inductor behave as short ckt.



$$I_1 = I_2 \Rightarrow 15/3 = 5 = I_1 + I_2$$

$$I_1 = I_2 = 1.5 \text{ A.}$$

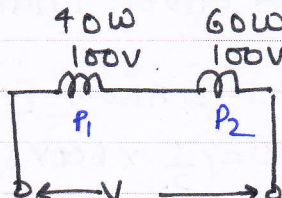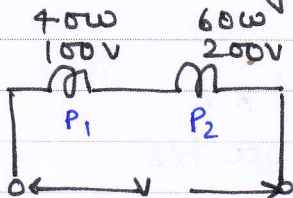Q.22. Following connection which give more brightness.



Ans (i) $R_1 = \frac{P}{I^2} = \frac{V^2}{P}$

$$R_1 = \frac{V_1^2}{P_1} = \frac{(100)^2}{40} = 250 \Omega$$

$$R_2 = \frac{V_2^2}{P_2} = \frac{(200)^2}{60} = 666.7 \Omega$$

$R_2 > R_1$; so $P_2 > P_1$. $\therefore P_2$ more bright

(iii) $R_1 = \frac{V_1^2}{P_1} = \frac{(100)^2}{40} = 250 \Omega$

$$R_2 = \frac{V_2^2}{P_2} = \frac{(100)^2}{60} = 166.66 \Omega$$

$R_1 > R_2$

$P_1 > P_2$

P_1 more bright.





* STEADY STATE AC CIRCUIT *

9784236981

SUBJECT - NETWORK TOPIC STEADY STATE
A.C. circuit.

P. No: 23

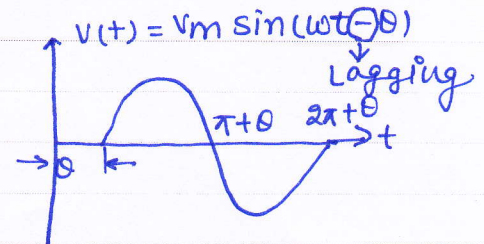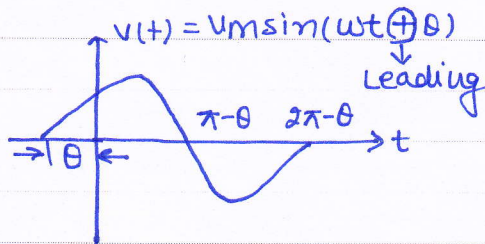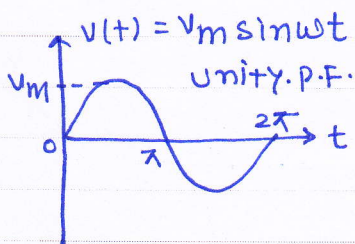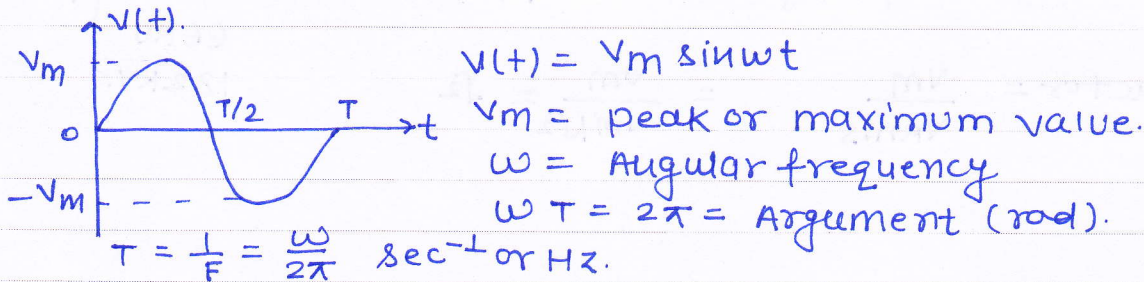- Advantage of sine waves:-
1. It is easy to handle mathematical problem like differential or integral, re write in term of sine function by Fourier Analysis.
 2. It is easy to generate in laboratory.



Rms value (Root mean SQUARE):-

1. Rms value is defined based on Heating effect of the waveform.
2. The voltage at which heat dissipation in AC ckt equal heat dissipation in DC ckt at equal resistance and time. ($W_{AC} = W_{DC} = I^2 R t$).

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 d\omega t} = \sqrt{\frac{1}{T} \int_0^T v^2 d\psi}$$

Average value:

1. It is based on charge transfer in ckt
2. the voltage at which charge transfer in AC circuit equal to charge transfer in DC circuit at same resistance and time. ($Q_{AC} = Q_{DC} = It$)
- *3. Find Avg. value of symmetric wave consider HALF cycle else used FULL cycle.
4. Average value of complete cycle of symmetric wave equal to zero.


→ To identify about shape of the waveform Form Factor and peak Factor concept are introduced.

$$\text{Form Factor} = \frac{V_{\text{rms}}}{V_{\text{avg}}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} = 1.11$$




$$\text{peak Factor} = \frac{V_m}{V_{\text{rms}}} = \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2}$$

Power system

11 KV }
 33 KV } F.F.
 66 KV }
 132 KV }

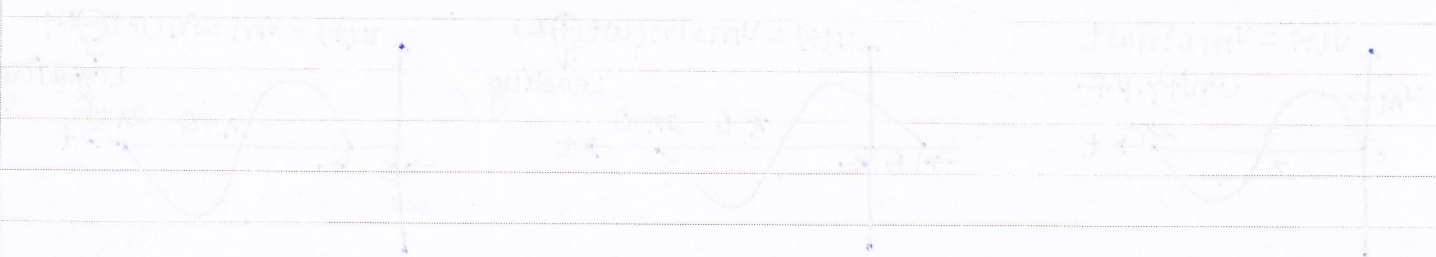

* A.C. SOURCE ACROSS RESISTOR *

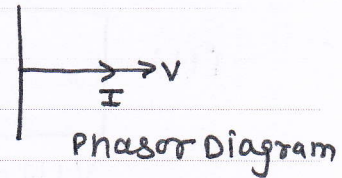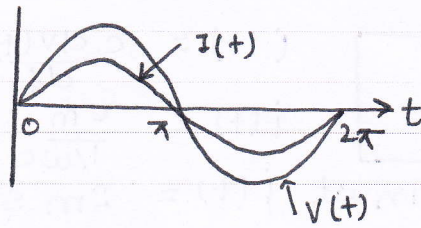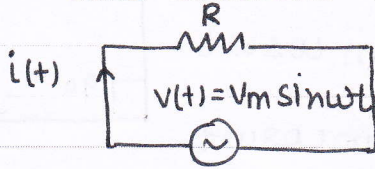

$$* P(t) = V(t) \cdot I(t) = V_m \sin \omega t \cdot I_m \sin \omega t = V_m I_m \sin^2 \omega t \quad \left\{ \sin^2 \omega t = \frac{1 - \cos 2\omega t}{2} \right.$$



$$* P(t) = \frac{V_m I_m}{2} [1 - \cos 2\omega t]$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P(t) \cdot dt = \frac{V_m I_m}{2}$$

$$* P_{avg} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{RMS} \cdot I_{RMS}$$

$$* \begin{aligned} F &= 50 \text{ Hz (wave)} \\ F_p &= 2 \times 50 = 100 \text{ Hz} \\ &\text{of power.} \end{aligned}$$

* AC SOURCE ACROSS INDUCTOR (L) *

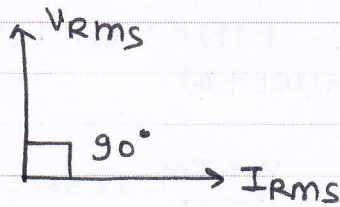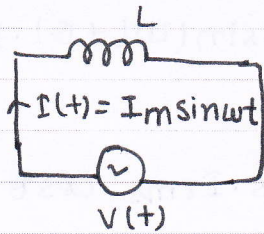

$$I(t) = I_m \sin \omega t \quad \text{--- (1)}$$

$$V(t) = L \frac{di(t)}{dt}$$

$$V(t) = \omega L I_m \cos \omega t$$

$$V = V_m \sin(\omega t + 90^\circ) \quad \text{--- (2)}$$

$$P(t) = V(t) \cdot I(t) = I_m \sin \omega t \cdot V_m \sin(\omega t + 90^\circ)$$

$$* P(t) = \frac{V_m \cdot I_m}{2} \sin 2\omega t$$


$$F = 50 \text{ Hz}$$

$$F_p = 100 \text{ Hz}$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P(t) \cdot dt \Rightarrow P_{avg} = 0$$

→ Phasor Diagram take Rms value. In series circuit I is reference and parallel circuit V take reference.


→ In ⊕ Half cycle inductor take Energy from source and ⊖ Half cycle taken source from inductor.

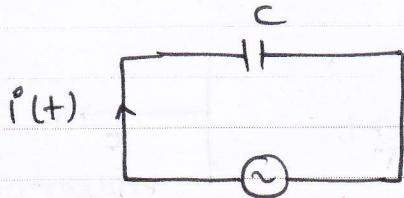* A.C. Source Across capacitor (C):

$$i(t) = \frac{C \frac{dV(t)}{dt}}{1} = \omega C V_m \cos \omega t$$

$$i(t) = \frac{V_m}{1/\omega C} \cos \omega t = I_m \cos \omega t$$
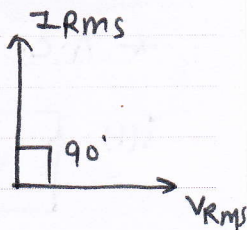
$$V(t) = V_m \sin \omega t \quad i(t) = I_m \sin(\omega t + 90^\circ)$$



$$P(t) = V(t) \cdot I(t) = v_m \sin \omega t \cdot I_m \cos \omega t = \frac{v_m I_m}{2} \sin 2\omega t$$

$$* \quad P(t) = \frac{v_m I_m}{2} \sin 2\omega t$$

$$* \quad \begin{matrix} F = 50 \text{ Hz} \\ F_p = 100 \text{ Hz} \end{matrix}$$

$$* \quad P_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} P(t) \cdot dt = 0$$

$$* \quad P_{\text{avg}} = 0$$

* POWER *

* Instantaneous power: - $P(t) = V(t) \cdot I(t) = V_m \sin(\omega t + \theta) \cdot I_m \sin \omega t$
 $P(t) = V_m I_m \sin \omega t \cdot \sin(\omega t + \theta)$

$$P_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} P(t) \cdot d\omega t = \frac{V_m \cdot I_m}{2} \cos \theta = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \theta$$

$$\text{power factor} = \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S} \Rightarrow \left\{ \begin{array}{l} \text{Voltage triangle: } V, V_R, V_X \\ \text{Impedance triangle: } Z, R, X \\ \text{Power triangle: } S, P, Q \end{array} \right\}$$

Voltage + Impedance + Power triangle.

* power factor angle indicated position of current phasor with respect to voltage phasor.

* (watt) P = Active power / True power / Real power / Avg. power / effective power


Q (VAR) = Volt Ampeare Reactive / Inductive Reactive power.

S (VA) = Volt Ampeare / Apperiant power / complex. power.

$$P = I^2 R = VI \cos \theta ; Q = I^2 X = VI \sin \theta , S = I^2 Z = VI^* = P + jQ$$

* $P_L = VI \cos \theta$ For unity p.f the losses are (VI) Low.

* R-L series circuit:

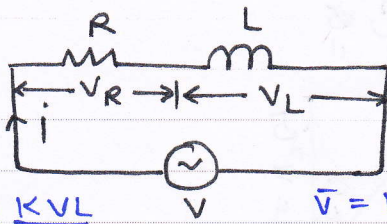


By KVL $\bar{V} = \bar{V}_R + j\bar{V}_L$

$V = V_R \angle 0^\circ + V_L \angle +90^\circ$


$I Z = I R + j I X_L$

$Z = R + j X_L$

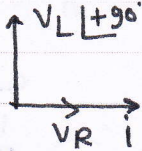


$V = \sqrt{V_R^2 + V_L^2}$

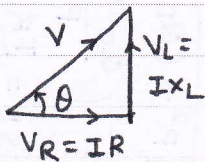$\theta = \tan^{-1} \left(\frac{V_L}{V_R} \right)$




$Z = \sqrt{R^2 + X_L^2}$

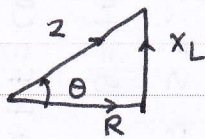$\theta = \tan^{-1} \left(\frac{X_L}{R} \right)$





$S = \sqrt{P^2 + Q^2}$

$\theta = \tan^{-1} (Q/P)$

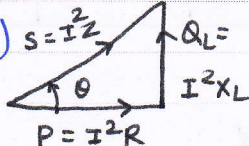

$\cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$ (power Factor) (Lead)

* RC-series circuit

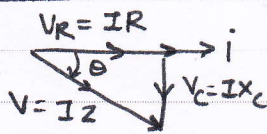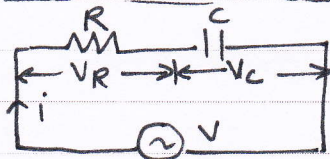

$V = V_R \angle 0^\circ + V_C \angle -90^\circ$

$I Z = I R - j I X_C$

$Z = R - j X_C$ (R)



$Z = \sqrt{R^2 + X_C^2}$

$\theta = \tan^{-1} \left(\frac{-X_C}{R} \right)$


$V = \sqrt{V_R^2 + V_C^2}$

$\theta = \tan^{-1} \left(\frac{-V_C}{V_R} \right)$

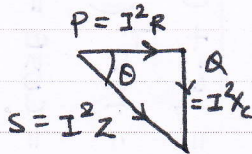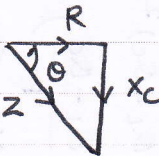$\theta = \tan^{-1} \left(\frac{-Q}{P} \right); \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$ (Lead)



* R-L parallel circuit.

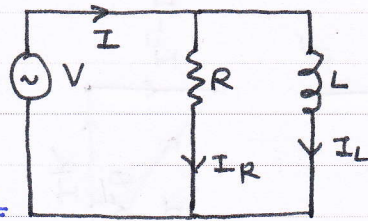

By KCL


$\bar{I} = \bar{I}_R + j\bar{I}_L$

$I = I_R \angle 0^\circ + I_L \angle -90^\circ$


$V/Z = V/R - jV/X_L$

$VY = VG - jVB_L$

$Y = G - jB_L$ (mho)

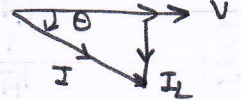

$V_G = IR$

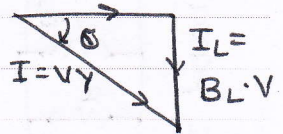

$I = \sqrt{I_R^2 + I_L^2}$

$\theta = \tan^{-1} \left(\frac{-I_L}{I_R} \right)$


$Y = \sqrt{G^2 + B_L^2}$

$\theta = \tan^{-1} \left(\frac{-B_L}{G} \right)$

$S = \sqrt{P^2 + Q^2}$



$\theta = \tan^{-1} \left(\frac{-Q}{P} \right)$

$P = V^2 G$

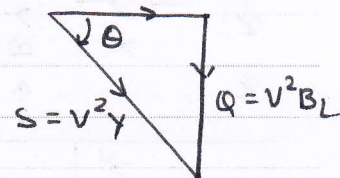

$\cos \theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S}$ (Lag) (power Factor)

* RC-Parallel circuit.

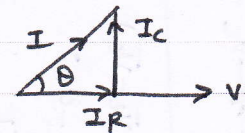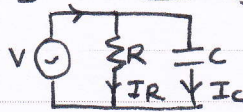

$I = I_R \angle 0^\circ + I_C \angle +90^\circ$

$V/Z = V/R + jV/X_C$

$VY = VG + jVB_C$

$Y = G + jB_C = \text{mho}$



$Y = \sqrt{G^2 + B_C^2}; \theta = \tan^{-1} \left(\frac{B_C}{G} \right)$

$I = \sqrt{I_R^2 + I_C^2}$


$\theta = \tan^{-1} \left(\frac{I_C}{I_R} \right)$

$\theta = \tan^{-1} (Q/P)$

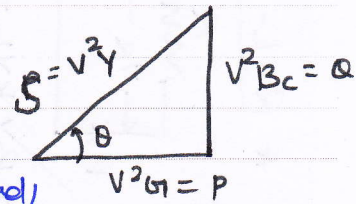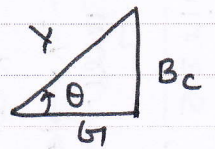$\cos \theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S}$ (Lead)



* R-L-C Series circuit

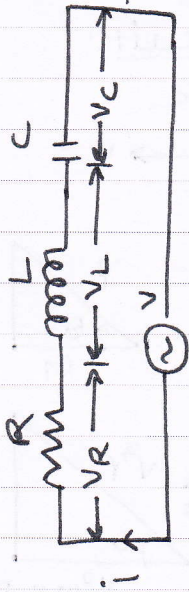

→ BY KVL ⇒ $\bar{V} = \bar{V}_R + j(\bar{V}_L - \bar{V}_C)$

$V = VR \angle 0^\circ + VL \angle 90^\circ + VC \angle -90^\circ$

$\bar{I}Z = \bar{I} [R + j(X_L - X_C)]$

→ $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$

→ $V = \sqrt{VR^2 + (VL - VC)^2}$

$\theta = \tan^{-1} \left(\frac{VL - VC}{VR} \right)$

→ $S = \sqrt{P^2 + (QL - QC)^2}$




$\theta = \tan^{-1} \left(\frac{QL - QC}{P} \right)$

→ P.F = $\cos \theta = \frac{VR}{V} = \frac{R}{Z} = \frac{P}{S}$


(i) $VL > VC$ (Lag.)

(ii) $VC > VL$ (Lead.)

(iii) $VL = VC$ (Unity)

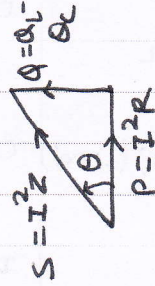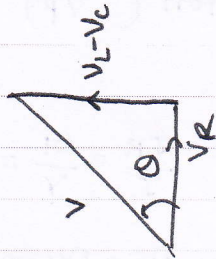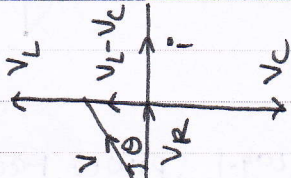

* R-L-C parallel circuit

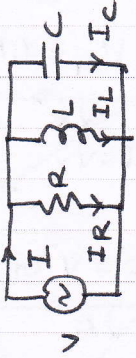

→ BY KCL ⇒ $\bar{I} = \bar{I}_R + j(\bar{I}_L - \bar{I}_C)$

$I = IR \angle 0^\circ + IL \angle -90^\circ + IC \angle 90^\circ$

$\frac{V}{Z} = \frac{V}{R} + j \frac{V}{X_C} - j \frac{V}{X_L}$

$Y = \frac{1}{Z} = \frac{1}{R + j(B_C - B_L)}$

→ $Y = \frac{1}{R + j(B_C - B_L)}$

$Y = \frac{1}{\sqrt{R^2 + (B_C - B_L)^2}}$

$\theta = \tan^{-1} \left(\frac{B_C - B_L}{R} \right)$

→ $I = \sqrt{IR^2 + (IL - IC)^2}$

$\theta = \tan^{-1} \left(\frac{IL - IC}{IR} \right)$

→ $S = \sqrt{P^2 + (Q_C - Q_L)^2}$





$\theta = \tan^{-1} \left(\frac{Q_C - Q_L}{P} \right)$

→ P.F = $\cos \theta = \frac{IR}{I} = \frac{P}{S}$








(i) $IC > IL$ (Lead)

(ii) $IL > IC$ (Lag.)

(iii) $IC = IL$ (Unity)

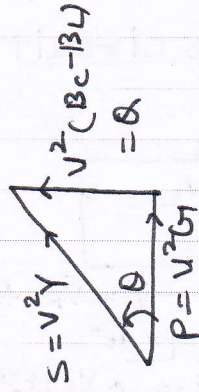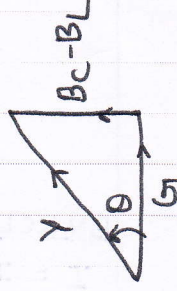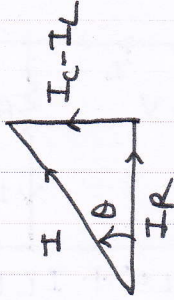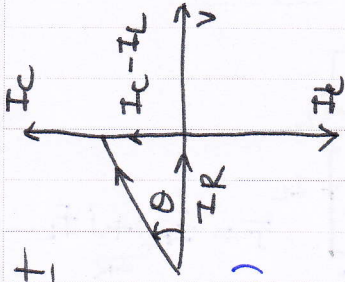

Q.1 Find the Average Value or Rms Value of given waveform.

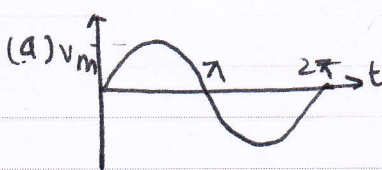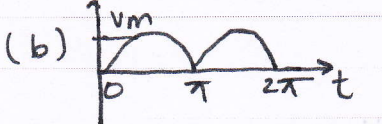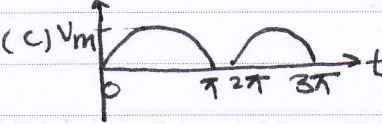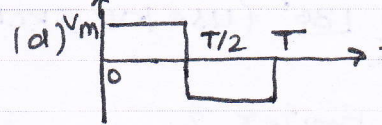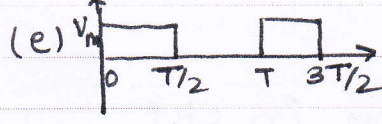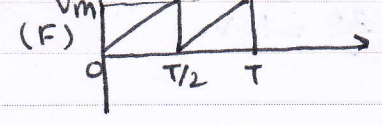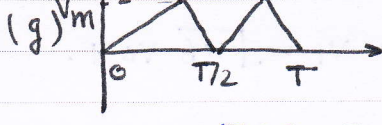(a) 	$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \cdot d\omega t$ $= \frac{2V_m}{\pi}$	$V_{RMS} = V_m / \sqrt{2}$	F.F & P.F F.F = 1.11 P.F = 1.41
(b) 	$V_{avg} = \frac{2V_m}{\pi}$	$V_{RMS} = V_m / \sqrt{2}$	F.F = 1.11 P.F = 1.41
(c) 	$V_{avg} = \frac{V_m}{\pi}$	$V_{RMS} = V_m / 2$	F.F = 1.57 P.F = 2
(d) 	$V_{avg} = V_m$	$V_{RMS} = V_m$	F.F = 1 P.F = 1
(e) 	$V_{avg} = \frac{V_m}{2}$	$V_{RMS} = V_m / \sqrt{2}$	F.F = $\sqrt{2}$ P.F = $\sqrt{2}$
(f) 	$V_{avg} = V_m / 2$	$V_{RMS} = V_m / \sqrt{3}$	F.F = $\frac{2}{\sqrt{3}}$ P.F = $\sqrt{3}$
(g) 	$V_{avg} = V_m / 2$	$V_{RMS} = V_m / \sqrt{3}$	F.F = $\frac{2}{\sqrt{3}}$ P.F = $\sqrt{3}$

$$\text{Form Factor} = \frac{V_{RMS}}{V_{avg}} ; \text{Peak Factor} = \frac{V_m}{V_{RMS}}$$

Q.2. Find Rms value of following function

$$V(t) = 3 + \sin 3t + \cos t$$


$$\text{Ans: } V_{RMS} = \sqrt{(3)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2} = \sqrt{10}$$

Q.3. Find power dissipation in the resistor at $V_{RMS} = V_m / \sqrt{2}$

$$\text{Ans: } P_{avg} = \frac{V_{RMS}^2}{R} ; P_{peak} = \frac{V_m^2}{R}$$

$$P_{avg} = \frac{(V_m / \sqrt{2})^2}{R} = \frac{V_m^2}{2R}$$

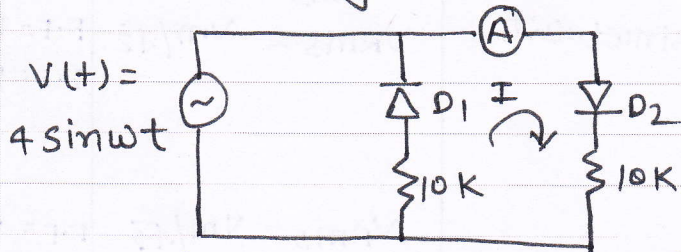Q.4. When the N/w is having ideal diode, resistor avg. value of indicating ammeter. Find Reading of Ammeter.



Aus:- It work Half Wave Rectifier

$$I_{av} = \frac{V_{avg}}{R} = \frac{V_m/\pi}{R} = \frac{4/\pi}{10K} = \frac{0.4}{\pi} \text{ mA.}$$


Q.5. $V(t) = 10 \sin(\omega t + 30^\circ)$ present in vector or phasor form?

Aus: Vector form: $\rightarrow 10 \angle 30^\circ$; phasor form $\rightarrow \frac{10}{\sqrt{2}} \angle 30^\circ$ (use KVL & KCL).

Q.6. $V = 10 \angle 30^\circ$; $i = 5 \angle 10^\circ$ Find complex power?

Aus:- $S = VI^* = 10 \angle 30^\circ \times 5 \angle -10^\circ = 50 \angle 20^\circ$

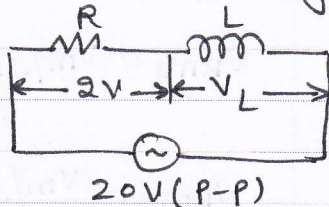Q.7. Find voltage across inductor shown in ckt





$$V_{(P-P)} = 20V. \quad V_m = \frac{20}{2} = 10V.$$

$$V = 10/\sqrt{2}$$

Aus:- $V = \sqrt{V_R^2 + V_L^2} \Rightarrow 10/\sqrt{2} = \sqrt{4 + V_L^2} \Rightarrow V_L = \sqrt{46} \text{ Volt.}$

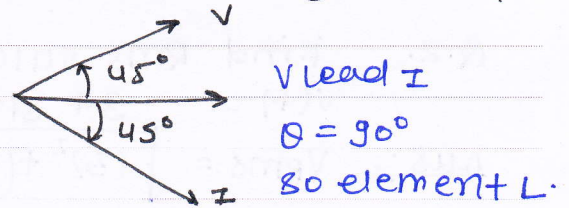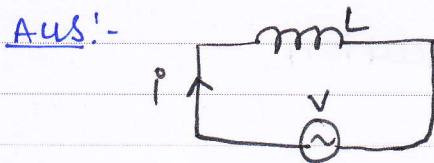Q.8. $V(t) = 9 \sin(t + 45^\circ)$; $I(t) = 3 \sin(t - 45^\circ)$

Find circuit element for given voltage and current equations:



$$X_L = \frac{V}{I} = \frac{9/\sqrt{2}}{3/\sqrt{2}} = 3; \quad \omega = 1$$

$$X_L = \omega L = 3$$

$$L \times 1 = 3 \Rightarrow L = 3H.$$

Q.9. Find circuit element for given voltage and current eqⁿ.

$$V(t) = 9 \sin(t + 30^\circ); I(t) = 3 \sin(2t + 60^\circ)$$

Ans: It is not possible to design the circuit element because frequency of voltage and current are unequal.


$$\omega_V = 1; \omega_I = 2; \omega_V \neq \omega_I$$

Q.10. Find Active and Reactive power by using voltage & current eqⁿ.

$$V(t) = 9 \sin(t + 30^\circ); I(t) = 3 \sin(t + 60^\circ)$$

Ans: Active power $P = VI \cos \theta$
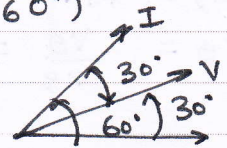
$$P = \frac{9}{\sqrt{2}} \times \frac{3}{\sqrt{2}} \cos 30^\circ = \frac{27\sqrt{3}}{4} \text{ Watt}$$



Reactive power $Q = VI \sin \theta$

$$Q = 9/\sqrt{2} \times 3/\sqrt{2} \times \sin 30^\circ = 27/4 \text{ VAR (Volt-Amp-Reactive).}$$

$$Z = V/I = 9/\sqrt{2} / 3/\sqrt{2} = 3 \Omega$$


$$\cos \theta = R/Z = R/3 = \cos 30^\circ \therefore R = 3\sqrt{3}/2 \Omega$$

$$Z^2 = X_c^2 + R^2 \Rightarrow 9 - 27/4 = X_c^2 \therefore X_c = 3/2 \Omega.$$

$$\text{Power } P = I^2 R = \left(\frac{3}{\sqrt{2}}\right)^2 \times \frac{3\sqrt{3}}{2} = \frac{27\sqrt{3}}{4} \text{ Watt} \therefore Q = I^2 X_c = \left(\frac{3}{\sqrt{2}}\right)^2 \times 3/2$$

$$Q = 27/4 \text{ VAR.}$$

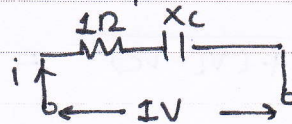Q.11 Find Angle of current with respect source voltage when power dissipation 500 mw.




$$P = I^2 R = \frac{V^2}{Z^2} \times R$$

$$500 \times 10^{-3} = \frac{1}{\sqrt{1+X_c^2}} \times 1 \Rightarrow X_c = 1 \Omega$$

$$\text{So } Z = R - jX_c = 1 - j1 \therefore \theta = \tan^{-1}(-X_c/R) = \tan^{-1}\left(-\frac{1}{1}\right) = -45^\circ$$

$$I = \frac{V}{Z \angle -45^\circ} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

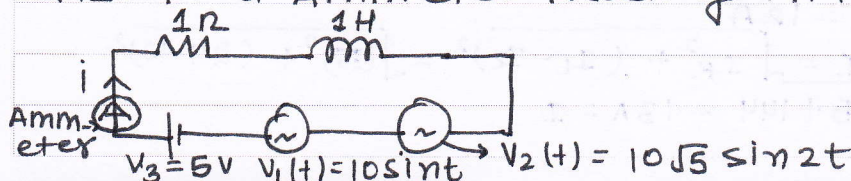Q.12. Find Ammeter Reading in the circuit shown



Ans: only 4 voltage source Active at a time.

For V_1 : $X_{L1} = \omega L \therefore V_1(t) = 10 \sin t \therefore \omega = 1 \therefore V_m = 10 \therefore V = 10/\sqrt{2}$

$$X_{L1} = 1 \times 1 = 1 \Omega$$

$$Z_1 = \sqrt{R^2 + X_L^2} = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$I_1 = \frac{V_1}{Z_1} = \frac{10}{\sqrt{2} \times \sqrt{2}} = 5A$$

For $V_2 \therefore V_2(t) = 10\sqrt{5} \sin 2t \therefore \omega = 2 \therefore V = 10\sqrt{5}/\sqrt{2}$

$$X_{L2} = \omega L = 2 \Omega$$

$$Z_2 = \sqrt{R^2 + X_L^2} = \sqrt{1^2 + 2^2} = \sqrt{5}$$


$$I_2 = \frac{V_2}{Z_2} = \frac{10\sqrt{5}}{\sqrt{2} \times \sqrt{5}} = \frac{10}{\sqrt{2}} A$$

For $V_3 = 5V, \omega = 0; X_L = 0$ so $Z = R = 1 \Omega$

$$I_3 = \frac{V_3}{R} = \frac{5}{1} = 5A$$

so Ammeter Reading $I = \sqrt{I_1^2 + I_2^2 + I_3^2} = \sqrt{(5)^2 + \left(\frac{10}{\sqrt{2}}\right)^2 + (5)^2} = 10A$

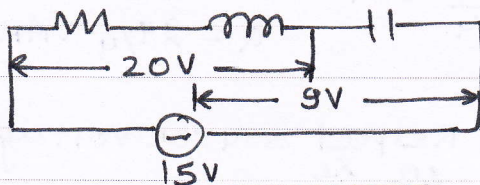Q.13. Find voltage across capacitor shown in fig.



$$\bar{V}_L - \bar{V}_C = 9V$$

$$\bar{V}_R + \bar{V}_L = 20V$$

$$\text{Ans: } V = \sqrt{V_R^2 + (V_L - V_C)^2} = 15 = \sqrt{V_R^2 + (9V)^2}$$

$$V_R = 12 \text{ VOLT.}$$

$$\therefore 20 = \sqrt{V_R^2 + V_L^2} \therefore \Rightarrow 20 = \sqrt{(12)^2 + V_L^2} \therefore V_L = 16 \text{ VOLT.}$$

$$(i) V_L > V_C$$

$$(ii) V_C > V_L$$


$$V_L - V_C = 9$$

$$V_C - V_L = 9$$

$$V_C = 16 - 9 = 7 \text{ VOLT.}$$

$$V_C = 9 + 16 = 25 \text{ VOLT}$$

Q.14. Find I_C & I OF the circuit shown:

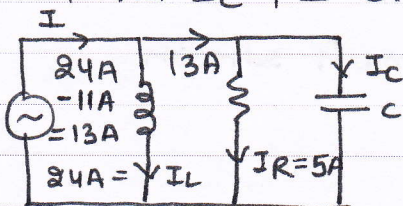


$$\text{Ans: } (13)^2 = \sqrt{I_R^2 + I_C^2} = \sqrt{25 + I_C^2}$$

$$I_C = 12A$$

$$\therefore I = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{(13)^2 + (24 - 12)^2} = \sqrt{25 + 144} = 13A = I$$

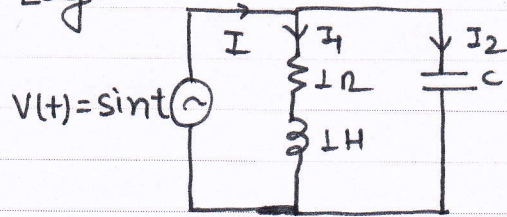Q.15. Find capacitance of capacitor then power factor of circuit is 0.8 Lag.



Ans $\rightarrow \omega = 1, \cos \theta = 0.8 ; X_L = \omega L = 1 \times 1 = 1 \Omega \therefore X_C = \frac{1}{\omega C} = \frac{1}{C}$

$$Y_{eq} = Y_1 + Y_2 = \frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} + \frac{j}{X_C}$$

$$Y_{eq} = \frac{1}{1+1} - j \frac{1}{1+1} + jC = \frac{1}{2} + j(C - \frac{1}{2})$$

$$\cos \theta = \frac{G}{\sqrt{G^2 + (B_C - B_L)^2}} = \frac{1/2}{\sqrt{(1/2)^2 + (C - 1/2)^2}} = 0.8 = \frac{8}{10}$$

$$(1/2)^2 + (C - 1/2)^2 = \frac{100}{64} \times \frac{1}{4} = \frac{100}{256}$$

$$(C - 1/2)^2 = \frac{100}{256} - \frac{1}{4} = \frac{9}{64}$$

$$C - 1/2 = \frac{3}{8}$$

$$C = \frac{3}{8} + \frac{1}{2} = \frac{7}{8} \text{ F.}$$

imp
CMT

A.C \rightarrow KVL, KCL \rightarrow Phasor sum

D.C \rightarrow KVL, KCL \rightarrow Airthmatic sum.

* THEOREM *

9784236981

SUBJECT -

TOPIC

P. No: 43.




* Superposition theorem : \rightarrow "In any linear bi-directional circuit having more than 1 independent source, the response in any one of the branch equal to algebraic sum of the response caused by individual sources while the rest of the source are replaced by its internal resistance".

NOTE

1. \rightarrow While applying superposition theorem depended source is replaced by neither open nor short circuit but independent source voltage replaced by short circuit but current source replaced by open circuit.
2. \rightarrow When network is having linear bidirectional elements with respect to homogeneity principle if excitation is multiplied by constant k . the response of each element also multiplied by k .
3. \rightarrow If the circuit have NO active independent source than voltage across it terminal = 0 = V_{th} .


point 1, 2 & 3 are same for all theorem.

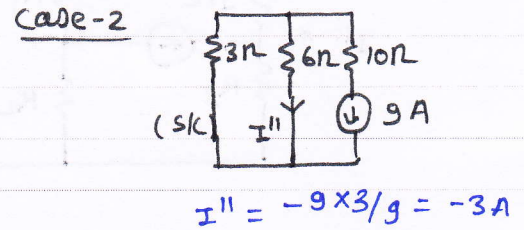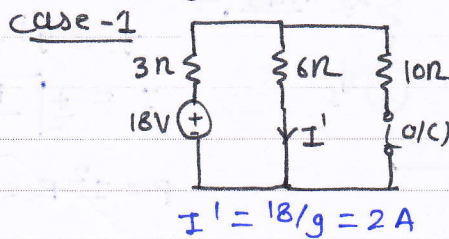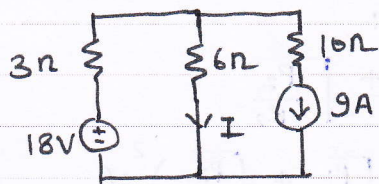Q.1. Find the value of I by superposition theorem: \rightarrow




So $I = I' + I'' = 3 - 3 = 0A$.


Q.2 Find V_x by superposition theorem:

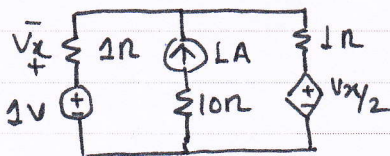

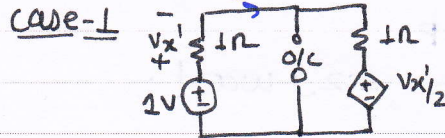$V_x = V_x'' + V_x' = \frac{2}{5} - \frac{2}{5} = 0$.



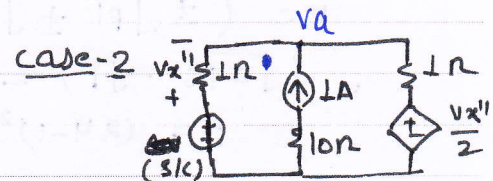$V_x' = I \times 1 = I$; $-1 + 2I + V_x'/2 = 0$
 $5/2 I = 1$; $I = \frac{2}{5} A = V_x'$



$V_x'' + V_x'' - V_x''/2 = 1$; $V_x'' = -2/5V$


Q.3 In the circuit if source voltage increased by 10%. Find variation of power in resistor R.

Ans:- case-1 NO.1 $\therefore V_s = V; R = R; P = V^2/R$

case-2 NO.2 $V_s = 1.1V; R = R; P = \frac{(1.1V)^2}{R} = 1.21P$

21% increased power.

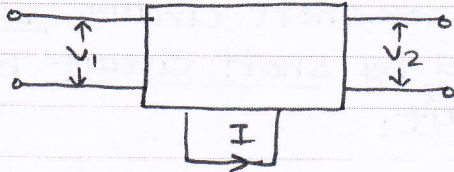Q.4. Find I when $V_1 = 10V; V_2 = -15V$.



V_1	V_2	I
2V	0	4A
0	3V	-2A


Ans:- It is superposition theorem because one source take at a time

$V_1 = 2V$ than $I_1 = 4A$ so $V_1 = 10V$ so $I_1 = 4 \times 5 = 20A$

$V_2 = 3V$ than $I_2 = -2A$ so $V_2 = -15V$ so $I_2 = -2 \times 5 = 10A$

total $I = I_1 + I_2 = 10 + 20 = 30A$.

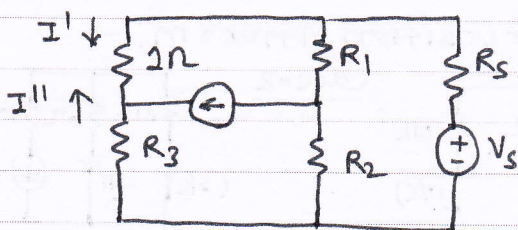Q.5. In the ckt shown power dissipation in the 1Ω resistor is 576 watt when voltage source acting alone and P.D in 1Ω resistor 1 watt when current source acting alone find total power dissipation in 1Ω resistor?



Ans:- $P = I^2 R; I = \pm \sqrt{P/R}$

$$I = I' + I''$$

$$I = \pm \sqrt{\frac{P_1}{R_1}} \pm \sqrt{\frac{P_2}{R_2}}$$

$$P = I^2 R = \left(\pm \sqrt{\frac{P_1}{R_1}} \pm \sqrt{\frac{P_2}{R_2}} \right)^2 \cdot R$$

When $R = R_1 = R_2$ so $= 1\Omega$

$$P = \left(\pm \sqrt{P_1} \pm \sqrt{P_2} \right)^2 \Rightarrow \sqrt{P^2} = \pm \sqrt{P_1} \pm \sqrt{P_2}$$

$$= \left(\sqrt{576} - \sqrt{1} \right)^2 = P$$

$$P = (24 - 1)^2 = 529 \text{ watt.}$$